

Karnaugh Map

for f_2

ab \ cd	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	0	0

$$= a b c d$$

for f_2

ab \ cd	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	0	0	1	1

$$= a \bar{b} c + a c \bar{d} = a c (b + \bar{d})$$

for f_1

ab \ cd	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	1	0	1
10	0	1	1	0

$$= \bar{a} b c + b c \bar{d} + a \bar{c} d + a \bar{c} d$$

$$= \underbrace{a d}_{\bar{A}} (\underbrace{\bar{c} + c}_{\bar{B}}) + \underbrace{b c}_{B} (\underbrace{\bar{d} + d}_{\bar{A}})$$


$$= A \oplus B = a d \oplus b c$$

for 10

cd	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	0	0	0

= b.d

Hand Drawn Gate Level Circuit

 

Console Output# run 1000ns

{a,b,c,d}=0000 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=0001 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=0010 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=0011 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=0100 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=0101 => {f3,f2,f1,f0} = 0001 -- TRUE
{a,b,c,d}=0110 => {f3,f2,f1,f0} = 0010 -- TRUE
{a,b,c,d}=0111 => {f3,f2,f1,f0} = 0011 -- TRUE
{a,b,c,d}=1000 => {f3,f2,f1,f0} = 0000 -- TRUE
{a,b,c,d}=1001 => {f3,f2,f1,f0} = 0010 -- TRUE
{a,b,c,d}=1010 => {f3,f2,f1,f0} = 0100 -- TRUE
{a,b,c,d}=1011 => {f3,f2,f1,f0} = 0110 -- TRUE
{a,b,c,d}=1100 => {f3,f2,f1,f0} = 0000 -- TRUE

$\{a,b,c,d\}=1101 \Rightarrow \{f_3,f_2,f_1,f_0\} = 0011$ -- TRUE

$\{a,b,c,d\}=1110 \Rightarrow \{f_3,f_2,f_1,f_0\} = 0110$ -- TRUE

$\{a,b,c,d\}=1111 \Rightarrow \{f_3,f_2,f_1,f_0\} = 1001$ -- TRUE


\$finish called at time : 800 ns : File

"C:/Users/omer/Desktop/Dersler/EHB436E/HW/03/Viv/project_3/project_3.srscs/sim_1/imports/Projectfiles/experiment3_tb.v" Line 52


RTL and Technology Schematics

No Timing and LOC Constraints

Technology Schematic

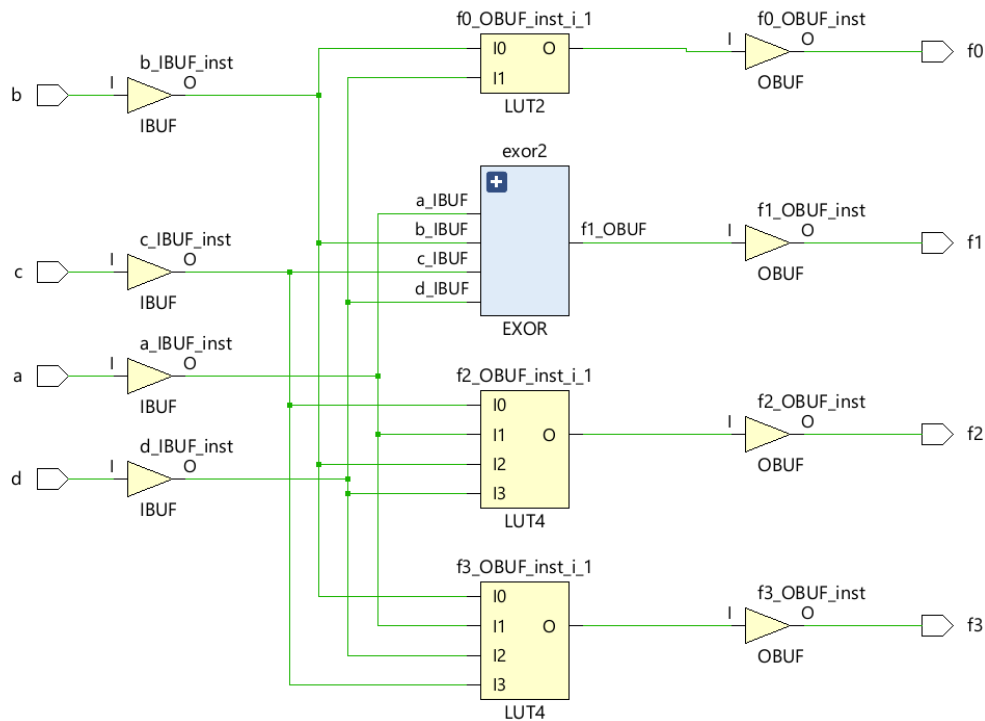

RTL Schematic

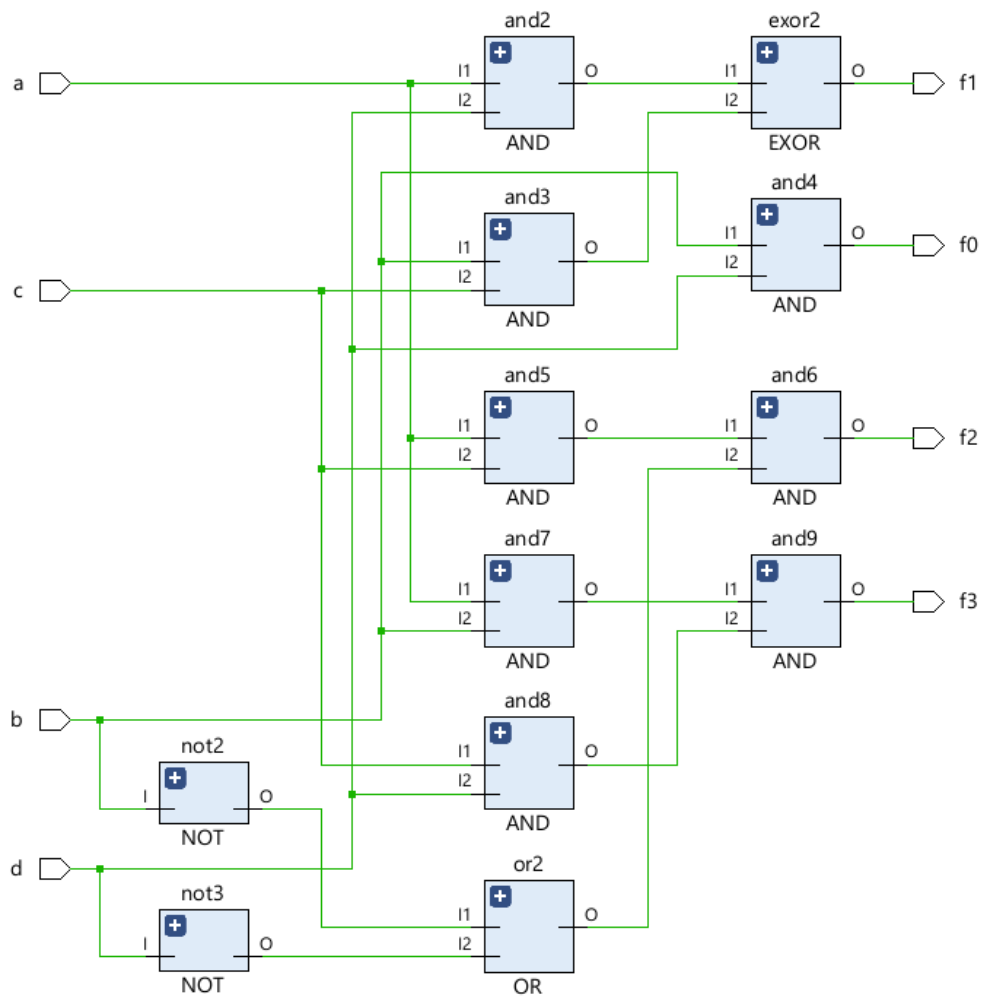


Combinational Delay Without Constraints

From Port	To Port	Max Delay ¹	Max Process Corner	Min Delay	Min Process Corner
a	f2	9.601	SLOW	2.992	FAST
a	f1	9.524	SLOW	2.9	FAST
d	f2	9.489	SLOW	2.910	FAST
b	f1	9.402	SLOW	2.851	FAST
c	f1	9.199	SLOW	2.728	FAST
a	f3	9.111	SLOW	2.809	FAST
c	f2	9.088	SLOW	2.720	FAST

Utilization Summary Without Constraints

Summary

Resource	Utilization	Available	Utilization %
LUT	5	63400	0.01
IO	8	210	3.81

 

With Time Constraint, No LOC Constraint


Maximum Combinational Delay with Timing Constraint

From Port	To Port	Max Delay	Max Process Corner
<input checked="" type="checkbox"/> a	<input checked="" type="checkbox"/> f1	8.997	SLOW
<input checked="" type="checkbox"/> c	<input checked="" type="checkbox"/> f2	8.744	SLOW
<input checked="" type="checkbox"/> a	<input checked="" type="checkbox"/> f2	8.720	SLOW
<input checked="" type="checkbox"/> b	<input checked="" type="checkbox"/> f2	8.633	SLOW
<input checked="" type="checkbox"/> d	<input checked="" type="checkbox"/> f1	8.610	SLOW
<input checked="" type="checkbox"/> b	<input checked="" type="checkbox"/> f1	8.562	SLOW
<input checked="" type="checkbox"/> b	<input checked="" type="checkbox"/> f0	8.512	SLOW

Utilization Summary with Timing Constraint



Summary

Resource	Utilization	Available	Utilization %
LUT	6	63400	0.01
IO	8	210	3.81

 

LUT usage is increased and that made circuit faster, using closer LUTs to the relevant port can make circuit faster

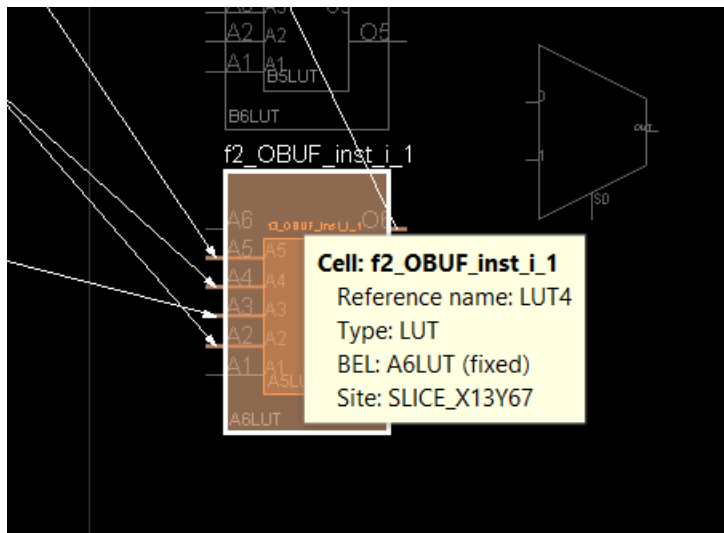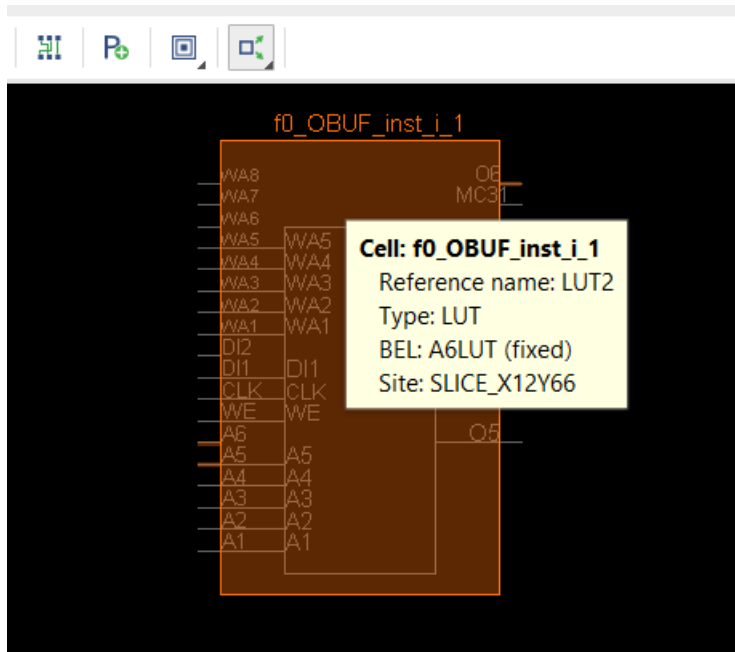With LOC constraint, No Timing Constraint



```
set_property LOC SLICE_X13Y67 [get_cells f2_OBUF_inst_i_1]
set_property LOC SLICE_X12Y66 [get_cells f0_OBUF_inst_i_1]
```

Combinational Delay with LOC constraint

The screenshot shows the 'Timing' tab in a software interface. The 'Combinational Delays' table is displayed with the following data:


From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process
c	f2	11.271	SLOW	4.12	Min Delay
d	f1	11.264	SLOW	3.721	FAST
d	f0	11.219	SLOW	3.757	FAST
d	f2	11.136	SLOW	4.065	FAST
b	f2	10.789	SLOW	3.923	FAST
a	f1	10.736	SLOW	3.487	FAST
b	f0	10.507	SLOW	3.470	FAST

With LOC and Time Constraints

The screenshot shows the 'Timing' tab in a software interface. The 'Combinational Delays' table is displayed with the following data:

From Port	To Port	Max Delay	Max Process Corner
d	f2	10.572	SLOW
c	f2	10.538	SLOW
d	f0	10.420	SLOW
b	f2	10.390	SLOW
a	f2	10.277	SLOW
d	f3	10.235	SLOW
c	f3	10.234	SLOW

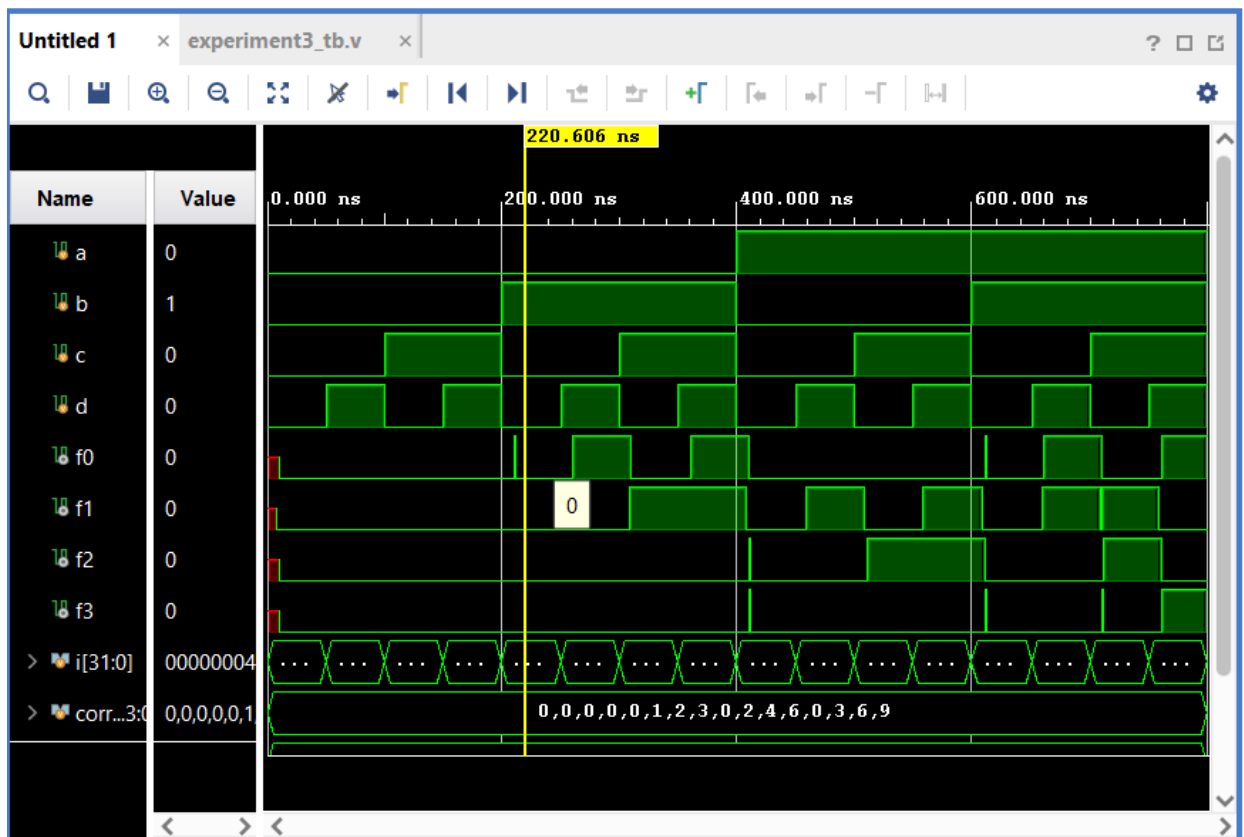It failed to make circuit delay with desired results because we fixed the locations of the LUTs so it could satisfy the conditions without changing LUTs locations



Difference between behavioural simulation and Post Implementation Timing Simulation


Because of the delays some unwanted results is occurring temporarily like when inputs are 0000 output must be 0000 but we see 1 at f0 for a short time period it is caused by different delay times between ports

Comparison

Each implementation has different delays, fastest one is the one that has only timing constraint because we did not fix any

LUT to a certain point so it changed their locations freely to meet the conditions of constraint file.

2 With Decoder

 


$$f_0 = \bar{a}b\bar{c}d + \bar{a}bcd + a\bar{b}\bar{c}d + abcd$$

$$f_1 = \bar{a}bc\bar{d} + \bar{a}bcd + a\bar{b}\bar{c}d + a\bar{b}cd \\ + ab\bar{c}d + abc\bar{d}$$


$$f_2 = a\bar{b}c\bar{d} + a\bar{b}cd + abcd$$

$$f_3 = abcd$$


Wave form of behavioral simulation

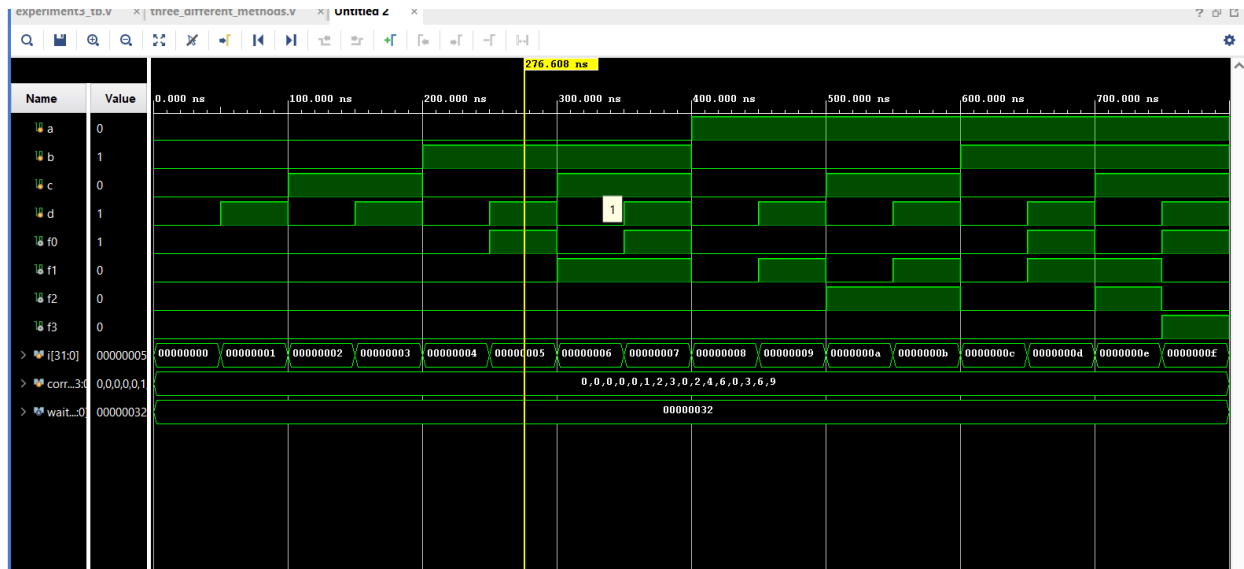

RTL schematic

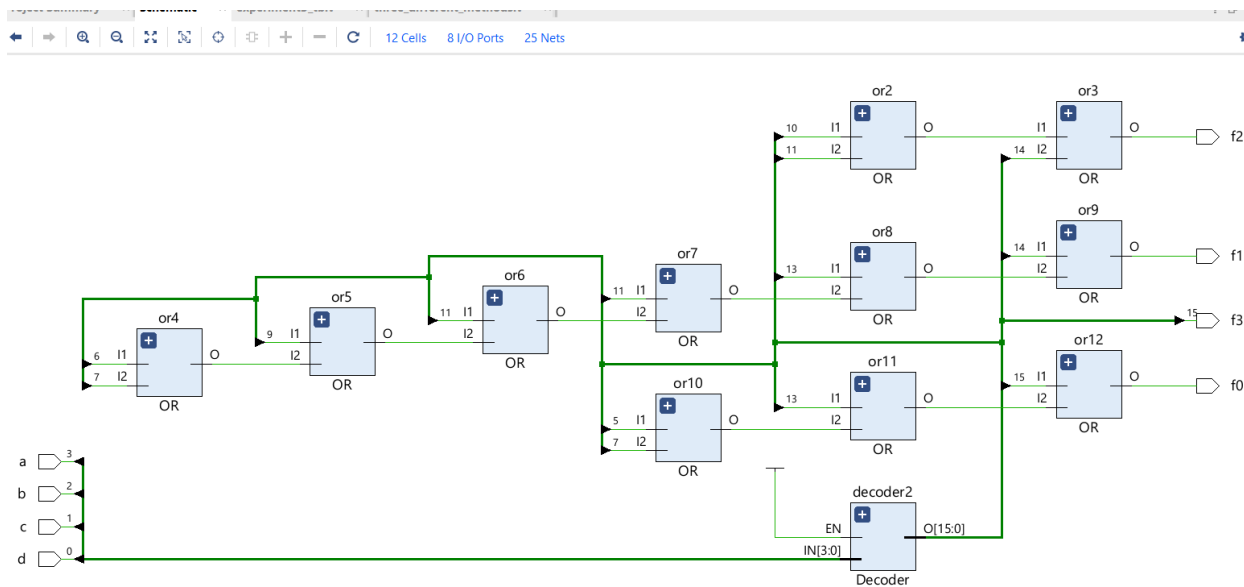

Technology Schematic

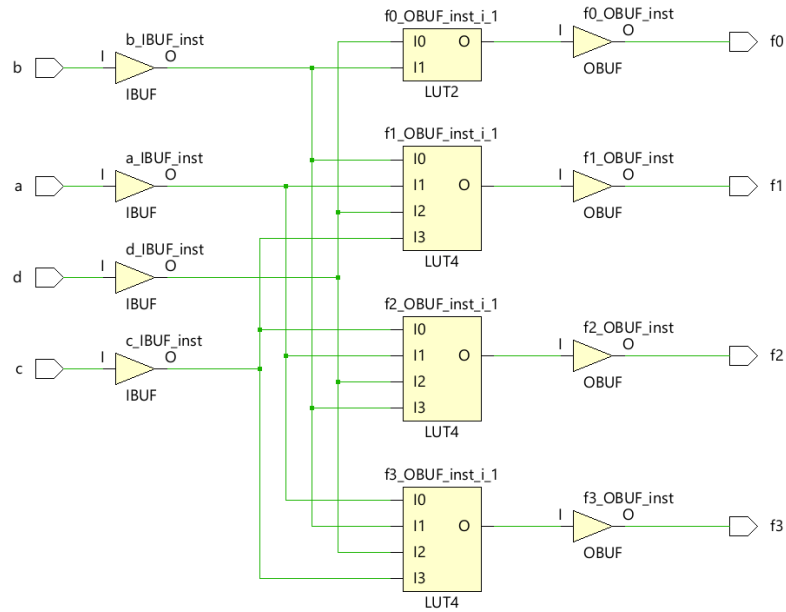


Combinational Delay

Combinational Delays

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
c	f2	14.493	SLOW	7.049	FAST
b	f0	14.143	SLOW	6.210	FAST
b	f2	13.729	SLOW	6.546	FAST
d	f0	12.479	SLOW	5.106	FAST
d	f2	12.051	SLOW	5.429	FAST
c	f1	11.864	SLOW	5.047	FAST
b	f1	11.100	SLOW	4.533	FAST
c	f3	10.942	SLOW	4.613	FAST
a	f2	10.533	SLOW	4.707	FAST
b	f3	10.188	SLOW	4.110	FAST
d	f1	9.425	SLOW	3.427	FAST
d	f3	8.498	SLOW	2.991	FAST
a	f1	7.910	SLOW	2.689	FAST
a	f3	6.998	SLOW	2.264	FAST

There is not different type of cell


Utilization

 

Comparison of Resource Usage Between Decoder and SSI Implementation

Design with decoder needs less process, in decoder part it just gives desired 1 to output, needs less process, that's why designing with decoder needs less resources.


Zoomed Device Layout

 


Combinational Delay With Timing Constraint

Tcl Console	Messages	Log	Reports	Design Runs	DRC	Power	Timing	×
<div>Q Combinational Delays</div>								
General Information		From Port	To Port	Max Delay	Max Process Corner			
Timer Settings		b	f0	11.007	SLOW			
Design Timing Summary		b	f1	10.582	SLOW			
Methodology Summary		c	f1	10.295	SLOW			
> Check Timing (4)		b	f3	10.188	SLOW			
Intra-Clock Paths		c	f3	9.968	SLOW			
Inter-Clock Paths		d	f2	9.798	SLOW			
> Other Path Groups		a	f2	9.785	SLOW			
User Ignored Paths		d	f3	8.837	SLOW			
> Unconstrained Paths		d	f0	8.207	SLOW			
Datasheet		a	f1	8.127	SLOW			
Input Ports Setup/Hold		a	f3	7.614	SLOW			
Output Ports Clock-to-out		d	f1	7.059	SLOW			
Combinational Delays		b	f2	5.748	SLOW			
Setup between Clocks		c	f2	5.650	SLOW			


3 Designing With Mux

 


Wave form of Behavioral Simulation

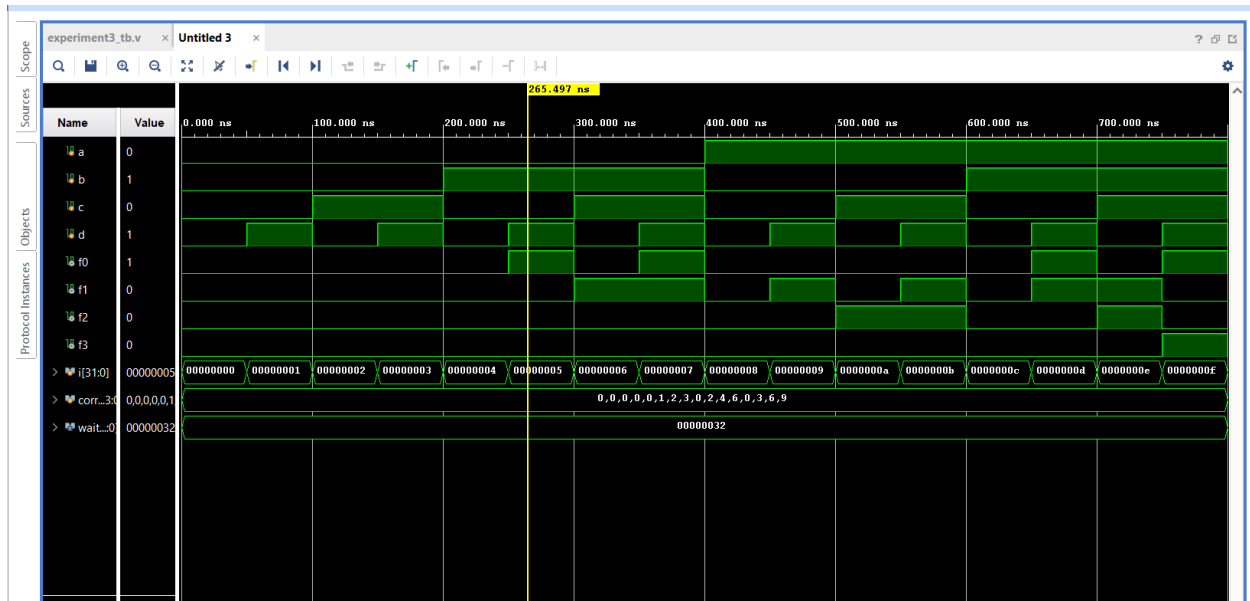

RTL Schematic

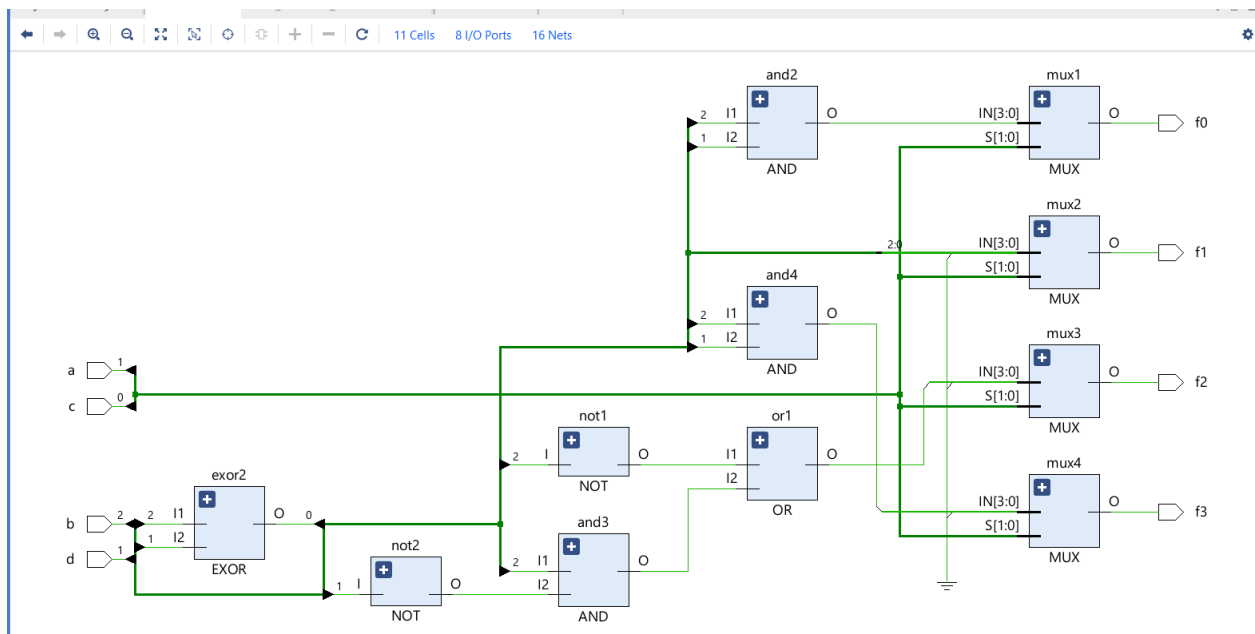

Technology Schematic


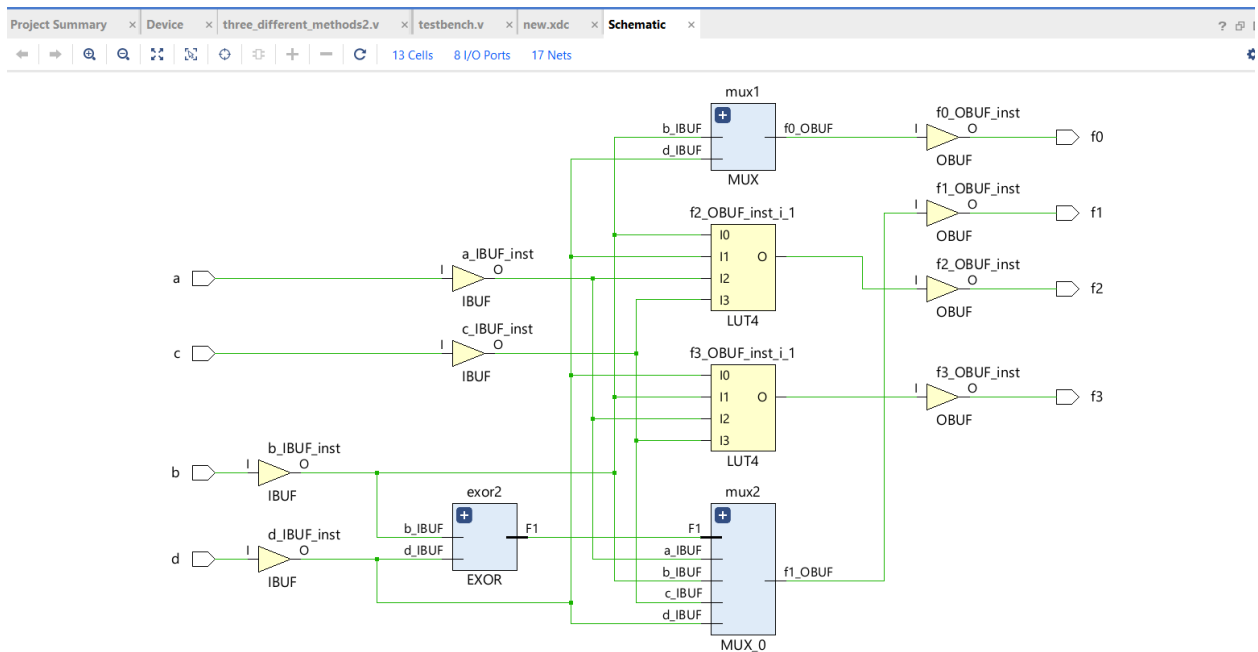


Combinational Delay

Timing						
Combinational Delays						
From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner	
b	f3	9.283	SLOW	2.857	FAST	
b	f0	9.045	SLOW	2.741	FAST	
b	f1	8.941	SLOW	2.666	FAST	
b	f2	8.854	SLOW	2.695	FAST	
c	f3	8.853	SLOW	2.694	FAST	
d	f3	8.777	SLOW	2.649	FAST	
c	f0	8.615	SLOW	2.578	FAST	

There is no difference in used primitive types

Utilization

 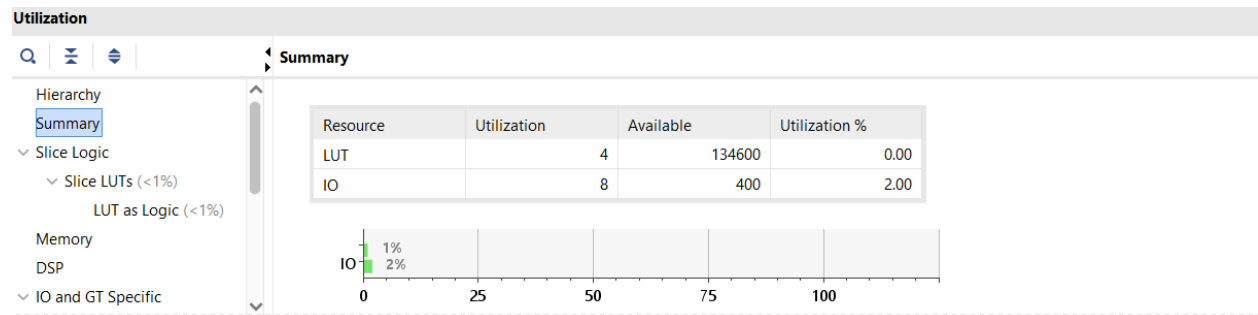

Comparison of three designs

Design with decoder is using least amount of resources because one decoder and 3 or is enough to implement the design, design with mux is in the middle because for every output we have to use one mux and some gates to their inputs, SSI is the worst case because we are using only gates that's why it is using more resources.

Combinational Delay with Time Constraint

From Port	To Port	Max Delay	Max Process Corner
c	f0	8.454	SLOW
b	f0	8.415	SLOW
d	f2	8.383	SLOW
c	f2	8.349	SLOW
b	f2	8.342	SLOW
c	f3	8.146	SLOW
c	f1	8.127	SLOW

4-)

It is 2-bit multiplier

Behavioral simulation is the simulation of our design.

Post Synthesis Functional Simulation is the simulation with synthesized netlists.

Post Implementation Functional Simulation is the simulation with using the elements on the board.

Post Implementation Timing Simulation is showing us that after implementing the design in to board, what happens with delays.

Design difficulty is MUX > Decoder >SSI

Coding difficulty SSI>MUX>Decoder

LUT usage SSI>MUX>Decoder

Path delays Decoder>SSI>MUX